

← ST 1: Network Theory



1

2

3

4

5

6

Filters

2




55sec

+1.0 -0.33



 Consider the circuit as shown in the figure below:



The Q-factor of the inductor is

1. $\sqrt{20}$

2. $\sqrt{18}$

3. $\sqrt{50}$

4. $\sqrt{49}$



← ST 1: Network Theory



Filters

Correct Answers Is: 1

35% got this right

SOLUTION**Concept:**

The quality factor is given by:

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

where Q = Quality factor

R = Resistance

L = Inductor

C = Capacitance

Calculation:

Given R= 5Ω, L= 1H, C= 2mF

$$Q = \frac{1}{5} \sqrt{\frac{1}{2 \times 10^{-3}}}$$

$$Q = \sqrt{\frac{1000}{2 \times 25}}$$

$$Q = \sqrt{20}$$

Was this solution helpful?



Hide Solution

Reattempt Mode



← ST 1: Network Theory



1

2

3


4

5


6

Filters

 
Simplify circuit given below into current source -



1.

 

2.

 

← ST 1: Network Theory



1

2

3


4

5


6

Filters

 Use source transformation in dotted region



The circuit can be redrawn as

 

Calculation of V_{TH} :

$$I_1 = (2-4)/(2+2) = -(1/2) \text{ A}$$

$$I_2 = (-6 - 3)/(3 + 1) = -(9/4) \text{ A}$$

$$V_{TH} = 2I_1 + 4 + I_2 + 3 = (2 \times -1/2) + 4 + (-9/4) + 3 = 15/4 \text{ V or } 3.75 \text{ V}$$



← ST 1: Network Theory



1

2

3

4

5


6

Filters

$$I_2 = (-0 - 3)/(3 + 1) = -(9/4) \text{ A}$$

$$V_{TH} = 2I_1 + 4 + I_2 + 3 = (2 \times -1/2) + 4 + (-9/4) + 3 = 15/4 \text{ V or } 3.75 \text{ V}$$


Calculation of R_{TH} :

 

$$R_{TH} = (2||2) + (3||1) = 7/4 \Omega$$

$$I_N = V_{TH} / R_{TH} = (15/4)/(7/4) = 15/7 \text{ A}$$

Norton equivalent circuit:

 

Was this solution helpful?



Hide Solution

Reattempt Mode



← ST 1: Network Theory



1

2

3

4

5

6

Filters

4




3sec

+1.0 -0.33



 Obtain the current 'I' in the network shown below -



1. $I = -12 \text{ A}$



2. $I = -9 \text{ A}$

3. $I = 12 \text{ A}$



4. $I = 9 \text{ A}$

Correct Answers Is: 1

47% got this right

Reattempt Mode



1

2

3

4

5


6

Filters

Concept:

Nodal analysis is a method that provides a general procedure for analyzing circuits using node voltages as the circuit variables. Nodal Analysis is also called the **Node-Voltage Method**.

Nodal Analysis is based on the application of Kirchhoff's Current Law (KCL).

 Calculation:

Use Nodal analysis at the node V_x

$$2 + (V_R/2) + (V_X - 3V_R)/5 = 0$$

$$\Rightarrow 2 + (V_R/2) + (4 + V_R - 3V_R)/5 = 0 \quad [\because V_X = 4 + V_R]$$

$$\Rightarrow 2 + (V_R/2) + (4 - 2V_R)/5 = 0$$

$$\Rightarrow V_R = -28 \text{ V}$$

$$I_R = V_R/2 = -28/2 = -14 \text{ A}$$

$$I = 2 + I_R = 2 + (-14) = -12 \text{ A}$$

← ST 1: Network Theory



1

2

3

4

5

6

Filters

5




42sec

+1.0 -0.33



The time constant of the network shown in the figure below is

 1. $2RC$ 2. $3RC$ 3. $\frac{RC}{2}$ 4. $\frac{2RC}{3}$ **Correct Answers Is: 4**

76% got this right

Reattempt Mode



← ST 1: Network Theory



2

3

4

5

6

7

Filters

7



25sec

+1.0 -0.33



Which of the following conditions holds good for a 2-port network to be reciprocal?

1. $Z_{11} = Z_{22}$

2. $H_{12} = H_{21}$


3. $Y_{12} = -Y_{21}$



4. $BC - AD = -1$

**Correct Answers Is: 4**

57% got this right

 SOLUTION

Reattempt Mode



2

3


4

5

6

7

Filters

 

A network is said to be reciprocal if the voltage appearing at port 2 due to a current applied at port 1 is the same as the voltage appearing at port 1 when the same current is applied to port 2.

Two Port Parameters	Condition for Symmetry	Condition for Reciprocal
Z Parameters	$Z_{11} = Z_{22}$	$Z_{12} = Z_{21}$
Y parameters	$Y_{11} = Y_{22}$	$Y_{12} = Y_{21}$
ABCD parameters	$A = D$	$\Delta T = AD - BC = 1$
H parameters	$\Delta h = h_{11}h_{22} - h_{12}h_{21} = 1$	$h_{12} = -h_{21}$

← ST 1: Network Theory




Filters

8 4min 19sec | +2.0 -0.66



 In the network given below, the output voltage V_o , when V_1 and I_1 are 10 V and 8 A respectively is:



V_1	I_1	V_o
5V	0A	3V
0V	2A	6V

1. 10 V

2. 30 V ✓

3. 24 V



6

7

8

9

10

11

 Filters**Correct Answers Is: 2**

45% got this right

SOLUTION

The voltage V_0 is contributed by the two sources present in the network.

\therefore Let $V_0 = \alpha V_1 + \beta I_1$

Case 1: $V_1 = 5 \text{ V}$, $I_1 = 0 \text{ A}$, $V_0 = 3 \text{ V}$

$$V_0 = \alpha V_1 + \beta I_1$$

$$\Rightarrow 3 = 5\alpha$$

$$\Rightarrow \alpha = 0.6$$

Case 2: $V_1 = 0 \text{ V}$, $I_1 = 2 \text{ A}$, $V_0 = 6 \text{ V}$

$$V_0 = \alpha V_1 + \beta I_1$$

$$\Rightarrow 6 = 0 + 2\beta$$

$$\Rightarrow \beta = 3$$

$$V_0 = 0.6 V_1 + 3 I_1$$

Now, $V_1 = 10 \text{ V}$, $I_1 = 8 \text{ A}$

$$V_0 = 0.6 (10) + 3 (8) = 30 \text{ V}$$

Was this solution helpful?

[Hide Solution](#)

Reattempt Mode



← ST 1: Network Theory



6

7

8

9

10

11

Filters


10

2sec

+2.0 -0.0



 The Thevenin equivalent voltage, V_{th} , in V across the load resistance (R_L) of the network shown below, is _____



Answer



Correct Answers Is: 27.9-28.1

19% got this right

SOLUTION

Reattempt Mode



6

7

8

9


10

11

Filters

SOLUTION

 By open circuiting the load terminals to evaluate the open circuit Thevenin voltage, the circuit becomes:



By applying KVL in the outer loop, we can write:

$$40 - 6I + 8 - 3I = 0$$

$$I = \frac{48}{9} = \frac{16}{3} \text{ A}$$

Since 4 A of current will flow across the 1 Ω resistance, by applying KVL to the left side of the circuit, we can write:

$$40 + 4 \times 1 - V_{th} - 3 \times \frac{16}{3} = 0$$

$$40 + 4 - V_{th} - 16 = 0$$

$$V_{th} = 28 \text{ V}$$

Was this solution helpful?



← ST 1: Network Theory



10

11

12

13

14

15

Filters


15

1sec

+2.0 -0.0



 For the parallel RLC circuit given below, the magnitudes of currents I_L and I_C are four times that of I_R .



The value of the inductance L is _____ (in μH)

Answer



Correct Answers Is: 3.1-3.2 22% got this right

SOLUTION

Reattempt Mode



11

12

13

14

15

Filters

Correct Answers Is: 3.1-3.2 22% got this right

SOLUTION

$$|I_L| = |I_C| = 4 |I_R|$$

\bar{I}_L and \bar{I}_C are equal in magnitude and opposite in phase, $\bar{I}_L + \bar{I}_C = 0$

$$\Rightarrow \bar{I} = \bar{I}_R$$

Therefore, the circuit is working under the resonance condition.

$$\text{Quality factor, } Q_o = \frac{|I_L|}{|I_R|} = \frac{4|I_R|}{|I_R|} = 4$$

For a parallel RLC circuit, the quality factor is

$$Q = R\sqrt{\frac{C}{L}}$$

From the given circuit diagram,

$$R = 5 \Omega, C = 2 \mu\text{F}$$

$$\Rightarrow 4 = 5\sqrt{\frac{2 \times 10^{-6}}{L}}$$

$$\Rightarrow L = 3.125 \mu\text{H}$$

Was this solution helpful?



1

2

3

4

5

6

Filters

1

20sec

+1.0 -0.33



In a 4-stage ripple counter, the propagation delay of a flip-flop is 100 ns. For a pulse width of the strobe as 100 ns, the maximum frequency at which the counter operates reliably is?

1. 1 MHz

2. 2 MHz



3. 500 MHz

4. 0.5 MHz

Correct Answers Is: 2

46% got this right

SOLUTION

For a n stage ripple counter the time period of clock is given by

Reattempt Mode



1

2

3

4

5

6

Filters

4. 0.5 MHz

Correct Answers Is: 2

46% got this right

SOLUTION

For a n stage ripple counter the time period of clock is given by

$$T_{CLK} \geq n t_{pd}$$

$$T_{CLK} \geq 4(100)$$

$$T_{CLK} \geq 400 \text{ nsec}$$

$$f_{CLK} \leq \frac{1}{400} \times 10^9$$

$$f_{CLK} \leq 2.5 \text{ MHz}$$

Hence from given options, the maximum frequency at which the counter operates reliably is 2 MHz

Was this solution helpful?



Hide Solution

Reattempt Mode



1

2

3

4

5

6

Filters


2

27sec

+1.0 -0.0



 The minimum number of flip flops required to implement the following state diagram which has 4 valid states.



Answer

**Correct Answers Is: 3-3**

58% got this right

SOLUTION

Reattempt Mode



1

2

3

4

5

6

Filters

Answer

**Correct Answers Is: 3-3**

58% got this right

SOLUTION

The state diagram shown in the figure has only four states. But a 3-bit counter is required to implement this sequence because the maximum binary count is seven.

So, number of flip flops required = 3

Was this solution helpful?



Hide Solution

Reattempt Mode



1

2

3

4

5

6

Filters

4

9sec

+1.0 -0.33



Three T flip flops are connected to form a counter. The maximum states possible for the counter will be:

1. 5

2. 3

3. 8



4. 7

Correct Answers Is: 3

72% got this right

SOLUTION

Concept:

For a counter with 'n' flip flops:

- The total number of states = 2^n (0 to $2^n - 1$)

Reattempt Mode



1

2

3

4

5

6

Filters

Concept:

For a counter with 'n' flip flops:

- The total number of states = 2^n (0 to $2^n - 1$)
- The largest number that can be stored in the counter = $2^n - 1$

To construct a counter with any MOD number, the minimum number flip flops required must satisfy:

$$\text{Modulus} \leq 2^n$$

Where n is the number of flip-flops and is the minimum value satisfying the above condition.

Calculation:

The total number of states required when $n = 3$:

$$2^3 \geq 8$$

The states will vary from (0 to 7)

So the maximum states possible for the counter will be 8.

Was this solution helpful?



Hide Solution

Reattempt Mode



1

2

3

4

5

6

Filters


5

0sec

+0.0 -0.0



 Consider the sequential circuit given below.



If the initial state of the flip-flops $Q_0 Q_1 Q_2$ is 101, which of the following is/are true?

**This question may have multiple correct answers*

1. The modulus of the counter is 3

2. The value of $Q_0 Q_1 Q_2$ after 6 clock pulses is 101



You missed this answer

3. The value of $Q_0 Q_1 Q_2$ after 5 clock pulses is 010



You missed this answer

4. Number of unused states are 5

1

2

3

4

5

6

Filters

4. Number of unused states are 5

Correct Answers Is: 2, 3

43% got this right

SOLUTION

From the given, sequential circuit,

$$J_0 = \bar{Q}_2, J_1 = Q_0, J_2 = Q_1$$

Clock pulse	Q_0	Q_1	Q_2	J_0	K_0	J_1	K_1	J_2	K_2
Initial	1	0	1	0	1	1	1	0	1
1	0	1	0	1	1	0	1	1	1
2	1	0	1						

After two clock pulses, it reaches its initial value. \therefore The Modulus of the counter will be 2.

$$\text{Number of unused states} = 8 - 2 = 6$$

After 5th clock pulse, $Q_0 Q_1 Q_2 = 0 1 0$

After 6th clock pulse, $Q_0 Q_1 Q_2 = 1 0 1$

Was this solution helpful?



Reattempt Mode



1

2

3

4

5

6

Filters

6

3sec

+2.0 -0.0



For the multistage counter arrangement of the given figure, determine the frequency of the output signal in Hz.



Answer



Correct Answers Is: 125-125 23% got this right

SOLUTION

Input frequency = 1 MHz.

4-bit binary ripple counter has $2^4 = 16$ states

Now, the frequency =

$$\frac{1 \times 10^6}{16} = 62.5 \times 10^3 \text{ Hz}$$



1

2

3

4

5

6

Filters

Answer



Correct Answers Is: 125-125 23% got this right

SOLUTION

Input frequency = 1 MHz.

4-bit binary ripple counter has $2^4 = 16$ states

Now, the frequency =

$$\frac{1 \times 10^6}{16} = 62.5 \times 10^3 \text{ Hz}$$

5-bit ring counter has 5 states.

$$\text{Now, the frequency} = \frac{62.5 \times 10^3}{5} = 12.5 \text{ kHz}$$

BCD counter has 10 states

$$\text{Now, the frequency} = \frac{12.5 \times 10^3}{10} = 1250 \text{ Hz}$$

5-bit Johnson counter has $2 \times 5 = 10$ states.

$$\text{The output frequency} = \frac{1250}{10} = 125 \text{ Hz}$$

Was this solution helpful?



5

6

7

8

9

10

Filters



7

2min 25sec

+2.0 -0.33



  The propagation delay of flip-flop and logic is zero, which of the following will be the waveform of output If Q_0 is reset to '0'



1. A

2. B



5

6

7

8

9

10

Filters

Concept:

Characteristic table of JK flip flop:

J	K	Q_{n+1}
0	0	Q
0	1	0
1	0	1
1	1	\bar{Q}


Truth Table of NAND gate:-

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

Analysis:-

From the circuit diagram, it is clear that the applied clock is a negative edged Trigger.

 Since, $J = K = 1$, the Next state will always be the complement to its previous state.



🔹 Filters

**This question may have multiple correct answers*

2. The FSM produces all possible states when x is 1.

!

You missed this answer

3. The FSM produces 3 possible states when x is 0.

3

4

5

6

7

8

Filters

$$D_A = Q_B \odot 1$$

$$D_B = Q_A \times$$

We will take two conditions for x, that is when $x = 0$ and when $x = 1$

$x = 0$

Q_A	Q_B	D_A	D_B	Q_A^+	Q_B^+
0	0	0	0	0	0
0	1	1	0	1	0
1	0	0	0	0	0
1	1	1	0	1	0

\therefore When $x = 0$, we can have only two out of the four possible states.

$x = 1$

Q_A	Q_B	D_A	D_B	Q_A^+	Q_B^+
0	0	0	0	0	0
0	1	1	0	1	0
1	0	0	1	0	1
1	1	1	1	1	1

\therefore When $x = 1$, we can have all four possible states.